

Experiment No: 04

Experiment Name: Verification of Kirchhoff's Current Law.

Course Code: EEE-1209

Course Title: Electrical Circuit lab

Submitted to:

Ms. Noshin Tahsin

Lecturer

Department of Computer Science and Engineering
Bangabandhu Sheikh Mujibur Rahman University
Kishoreganj, Bangladesh

Mr. Md. Sabab Zulfiker

Lecturer

Department of Computer Science and Engineering
Bangabandhu Sheikh Mujibur Rahman University
Kishoreganj, Bangladesh

Group-02:

Submitted By:


Names	ID No
Md. Sabbir Mia	202122104017
Amir Hamja Seman	202122104018
Md. Reduanur Rahman Rifat	202122104020
Md. Ehasan Mahmud	202122104026



Date of Submission: 01/11/2023

Department of Computer Science and Engineering,
Bangabandhu Sheikh Mujibur Rahman University
Kishoreganj, Bangladesh

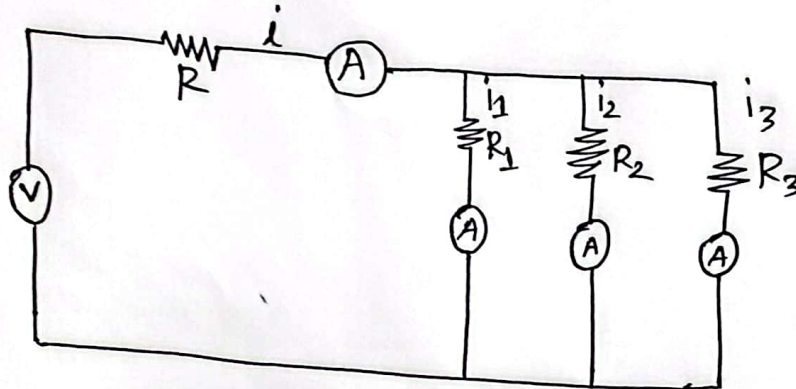Experiment name: Verification of KCL (Kirchoff's Current Law)



Data Table:

Observation	Voltage	Actual current (I)	I_1	I_2	I_3	$I_{\text{total}} = I_1 + I_2 + I_3$	Error	Error (%)
1	10V	5.9	1	4.7	0.1	5.8	0.1	1.69%
2	12V	6.9	1.1	5.5	0.2	6.7	0.2	2.89%

Group Member:

1. Md. Subbir Mia (202222208029)
2. Amir Hamja Berman (202222208028)
3. Md. Reduanur Rahman Rifat (202222208020)
4. Md. Ehasan Mahmud (202222208026)

স্বাক্ষরিত তারিখ
২০২২-০২-০৬

Experiment name: Verification of KCL (Kirchhoff's current Law)

Theory: The algebraic sum of the currents meeting at a node is equal to zero.


Required Equipment:

1. RPS (Regular power supply)
Range (0-30V) & Quantity 2
2. Resistance
Range (1K Ω , 4.7K Ω , 30K Ω , 6K Ω) &
Quantity 4.
3. Ammeter
Range (0-30mA) MC &
Quantity 3.
4. Voltmeter
Range (0-30V) MC &
Quantity 3.
5. Breadboard & wires.

Precautions:

1. Voltage control knob should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position.

Circuit Construction: circuit (KCL)

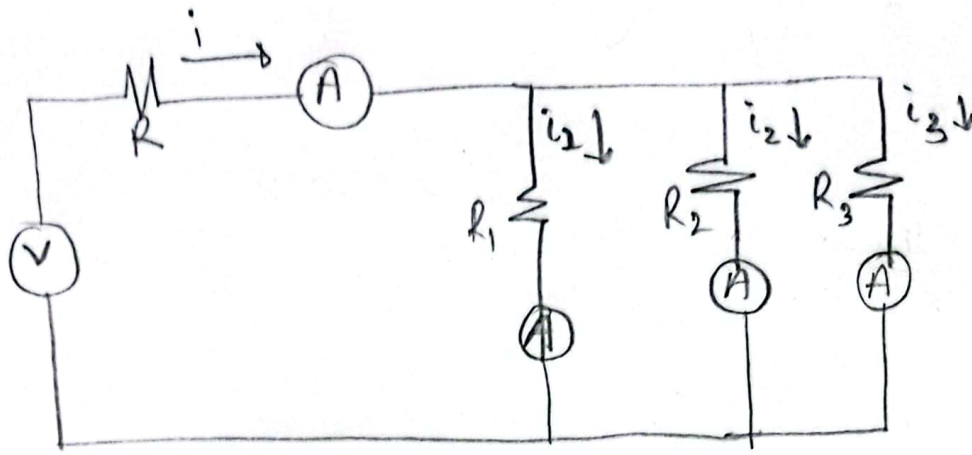

Procedure of KCL:

1. Give the connections as per the circuit diagram.
2. Set a particular value in RPS.
3. Note down the corresponding ammeter reading.
4. Repeat the same for different voltages.

KVL - Theoretical Values:

Observation	Voltage	Actual Current I_A (mA)	I_1 (mA)	I_2 (mA)	I_3 (mA)	$I = I_1 + I_2 + I_3$ (mA)	Error $(I_A - I)$
1	10V	5.6	4.5	0.9	0.1	5.5	0.1
2	12V	6.8	5.4	1.1	0.1	6.6	0.2

Result: From the data table, we find that current through different paths was different. Now we are going to test some of these data.

Sl. No	I_A	$I = I_1 + I_2 + I_3$
1	5.6	5.5
2	6.8	6.6

From the table, we can see that $I_1 + I_2 + I_3$ value is always near I_A .

Conclusion!

From the result section, we can see that current entering and exiting were the same. The algebraic sum of all currents entering and exiting a node was zero.

From this, we can say that Kirchhoff's current law is true in real world.