
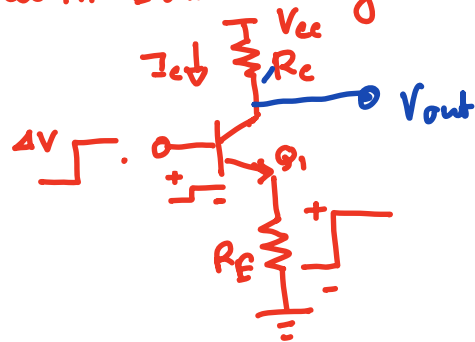


CE stage with Emitter Degeneration

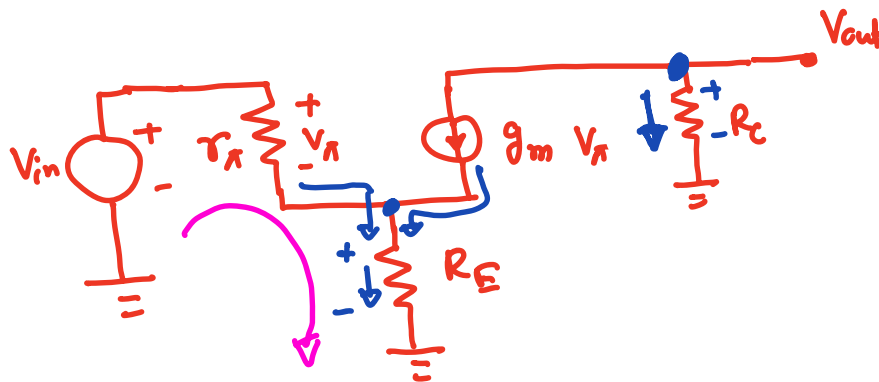

$$I_c = I_s \exp \frac{4V_{BE}}{V_T}$$



$$A_V = \frac{V_{out}}{V_{in}}$$

KCL @ output node

$$g_m V_\pi + \frac{V_{out}}{R_C} = 0$$

$$\therefore g_m V_\pi = - \frac{V_{out}}{R_C}$$

$$\therefore V_\pi = - \frac{V_{out}}{g_m R_C} \quad \text{--- (1)}$$

$$V_{RE} = \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) R_E \quad \text{--- (2)}$$

$$V_{in} = V_\pi + V_{RE}$$

$$= V_\pi + \left(\frac{V_\pi}{r_\pi} + g_m V_\pi \right) R_E \quad \text{[using eq 2]}$$

$$= V_{\pi} \left[1 + \left(\frac{1}{r_{\pi}} + g_m \right) R_E \right]$$

$$\Rightarrow V_{in} = - \frac{V_{out}}{g_m R_C} \left[1 + \left(\frac{1}{r_{\pi}} + g_m \right) R_E \right]$$

using eqⁿ 1

$$\Rightarrow \frac{V_{out}}{V_{in}} = - \frac{g_m R_C}{1 + \left(\frac{1}{r_{\pi}} + g_m \right) R_E}$$

$$\beta \gg 1, \quad g_m \gg 1/r_{\pi}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{- g_m R_C}{1 + g_m R_E}$$

$$= \frac{- g_m R_C}{g_m (1/g_m + R_E)}$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_C}{\frac{1}{g_m} + R_E}$$

without degeneration $R_E = 0$

$$\therefore \frac{V_{out}}{V_{in}} = - g_m R_C$$

Example 5.22, 5.23


Input Impedance:

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$

Output Impedance:

$$R_{out} = R_c$$

Common - Base Topology

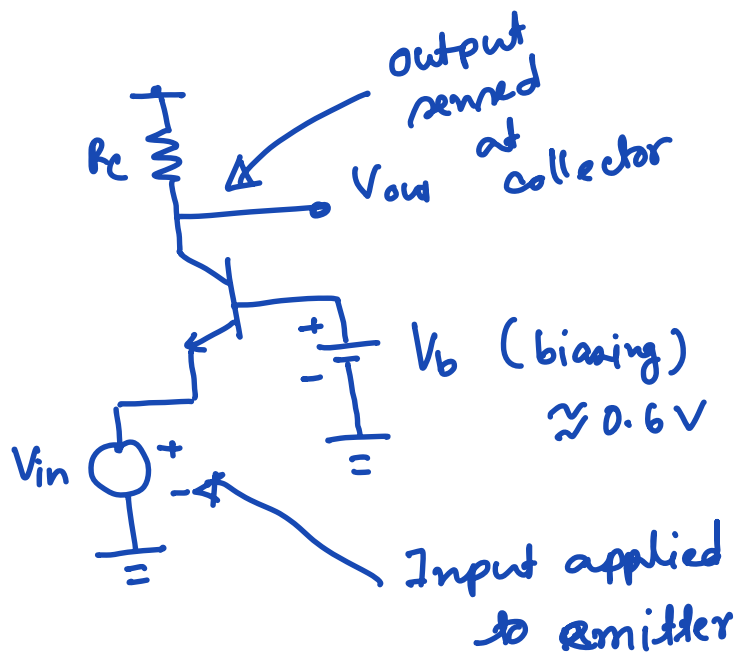

Voltage gain:

$$A_v = g_m R_c$$

$$g_m = \frac{I_c}{V_T}$$

Input impedance:

$$R_{in} = \frac{1}{g_m}$$


Output Impedance:

$$R_{out} = R_c \text{ if } V_A = \infty$$

or $R_{out} = R_c \parallel r_o \text{ if } V_A \neq \infty$

Example 5.42 (Tough problem)
10 marks.

Common collector (or emitter follower)

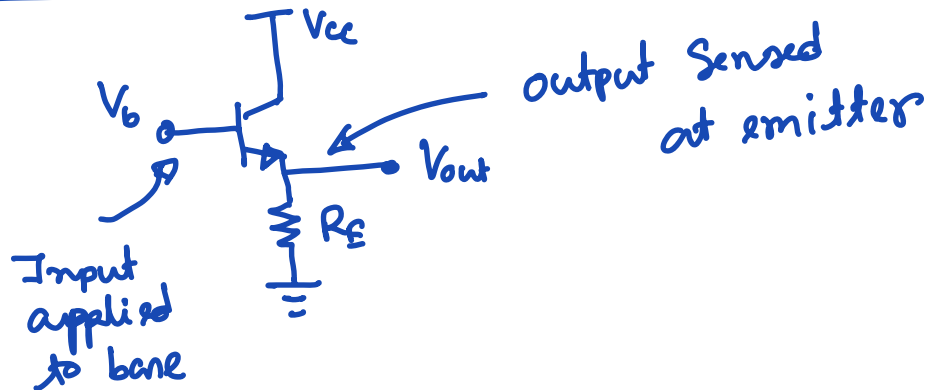

$$A_v = \frac{R_E}{R_E + \frac{1}{g_m}}$$

$$R_E \gg \frac{1}{g_m}$$

$$A_v < 1$$

Example 5.43 , Example 5.45