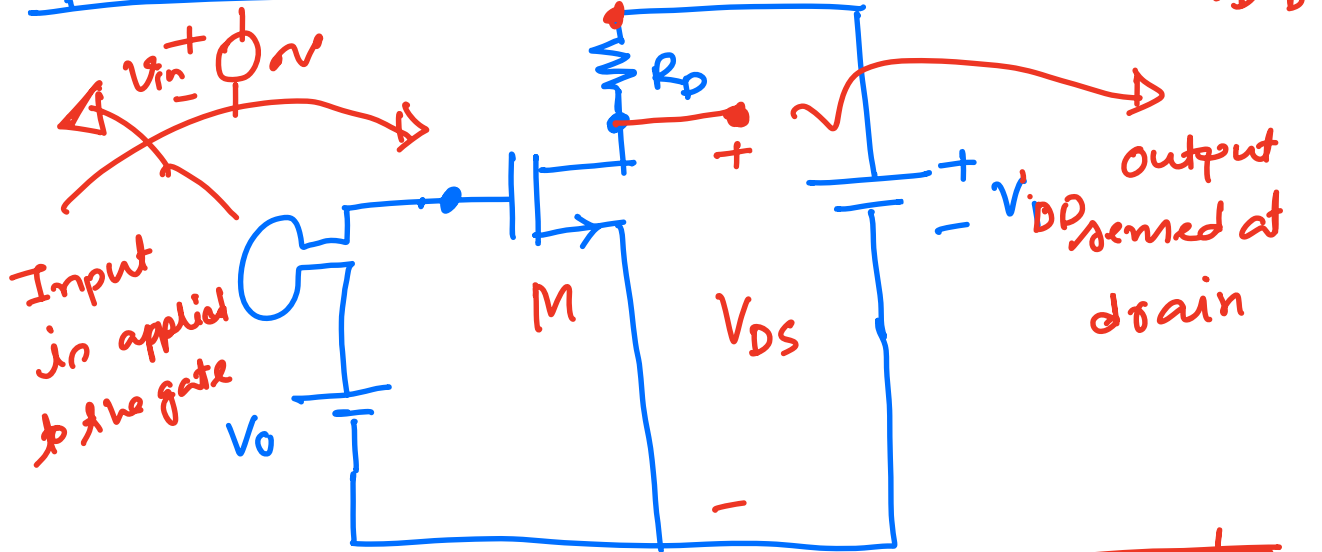


CMOS Amplifier

Common source stage




AV


For M_1 to maintain sat:

$$V_{DS} > V_{GS} - V_{th}$$

$$\Rightarrow V_{DD} - I_D R_D > V_{GS} - V_{th}$$

Small-signal Model.

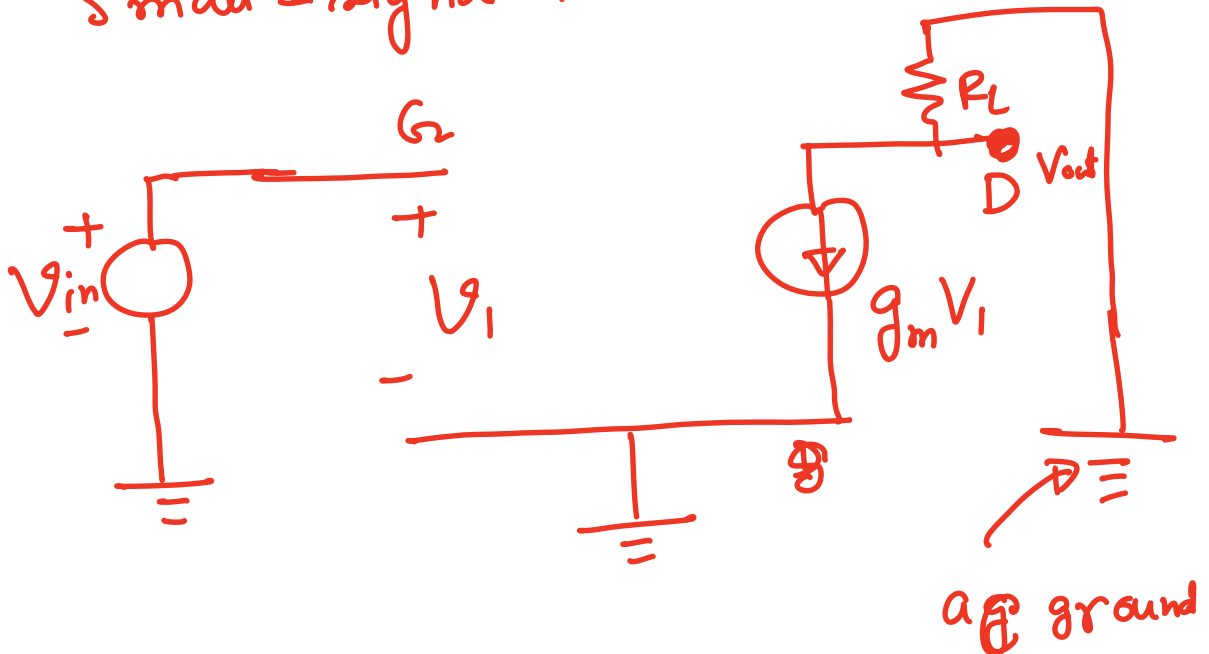

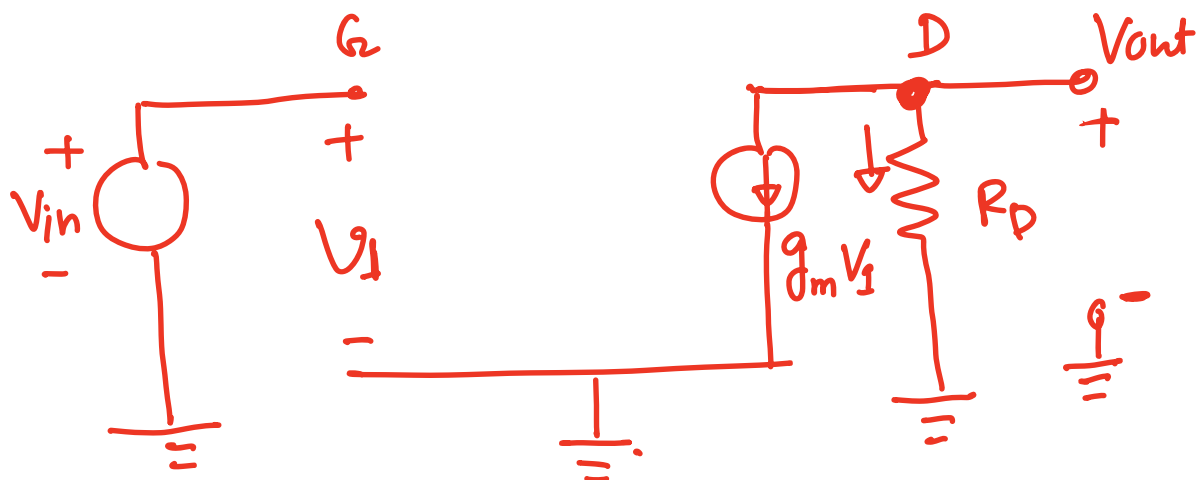

$$V_1 = V_{in}$$

$$g_m V_1 = g_m V_{in}$$

KCL @ node D,

$$g_m V_{in} + \frac{V_{out}}{R_D} = 0$$

$$\therefore \frac{V_{out}}{V_{in}} = -g_m R_D$$

$$\therefore \boxed{A_v = -g_m R_D}$$

when $\lambda = 0$

$A_v = -g_m \times (\text{total resistance tied between drain and ac ground})$

* Q: Draw the circuit diagram of the CS stage and find the small signal gain (Consider $\lambda = 0$)



Example 7.4

$$\gamma \neq 0$$

$$A_v = -g_m(R_D || r_o)$$


CS stage with current-source Load

Realization of current source:

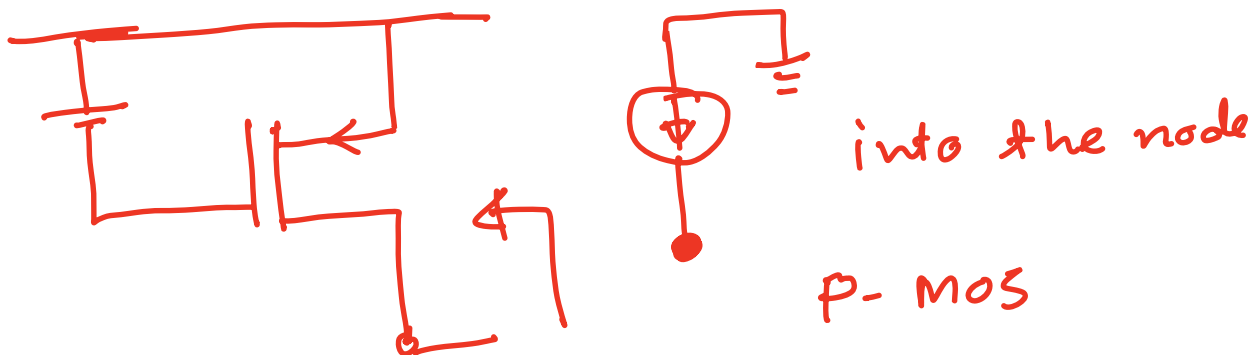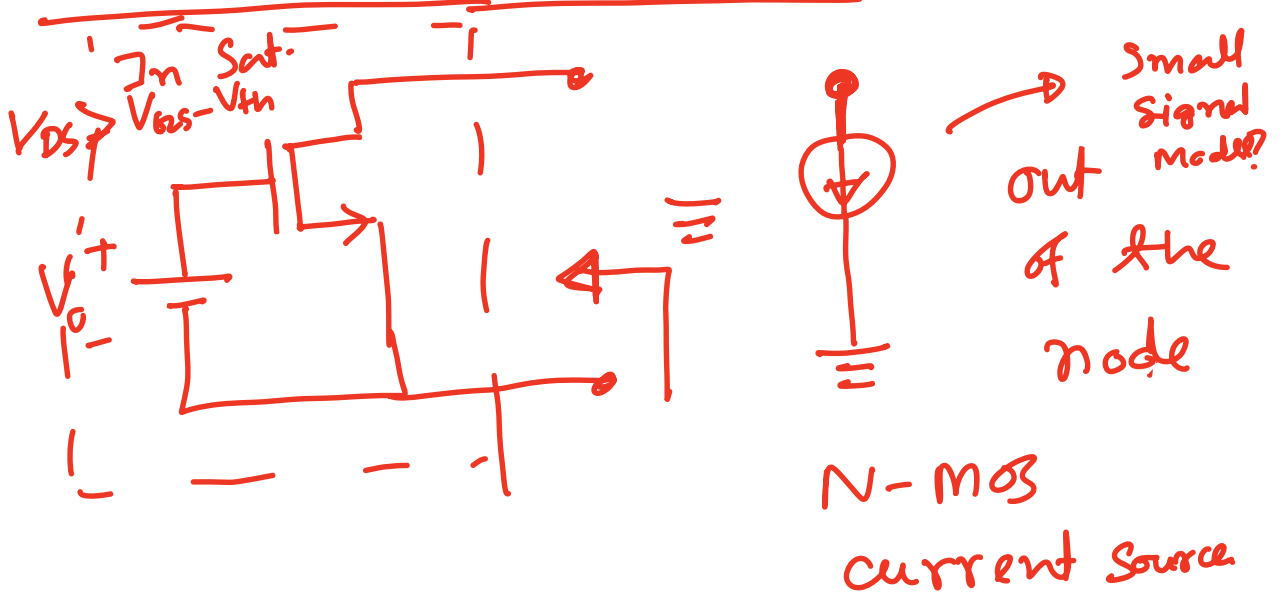


Small signal model of MOS current




Source:

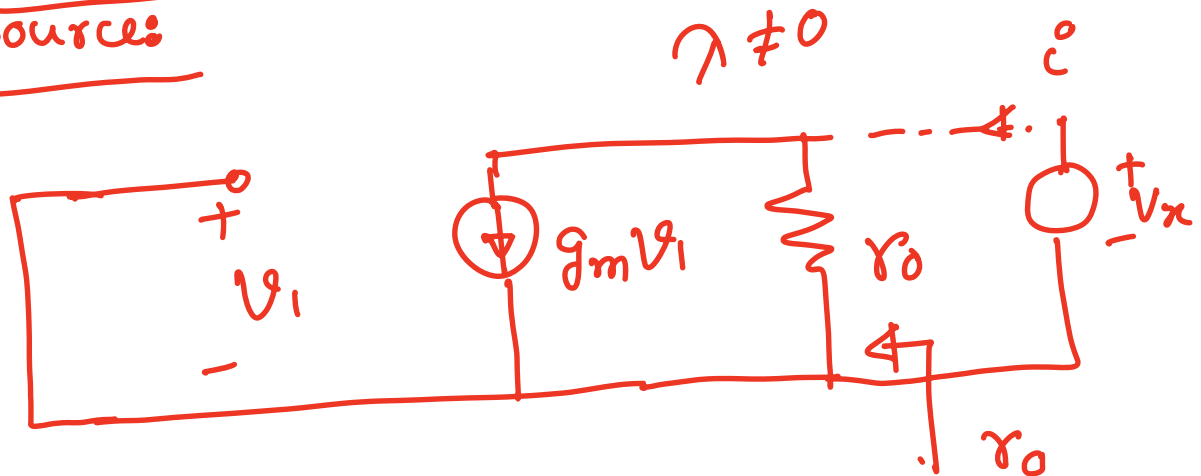


$$\frac{v_n}{i_n} = r_o$$

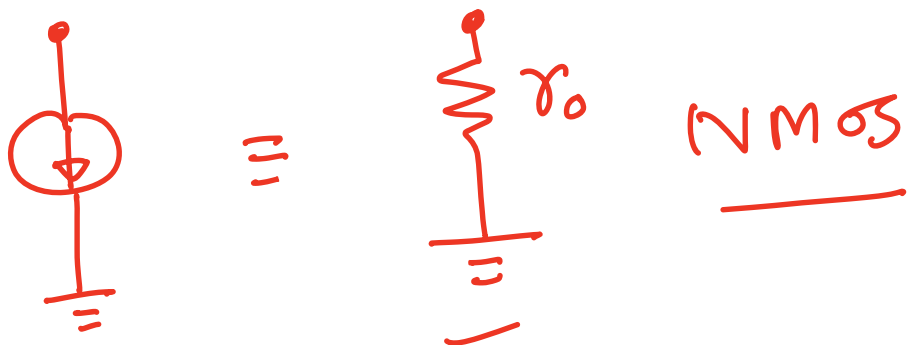No small signal model of MOS current source (if $\lambda \neq 0$)



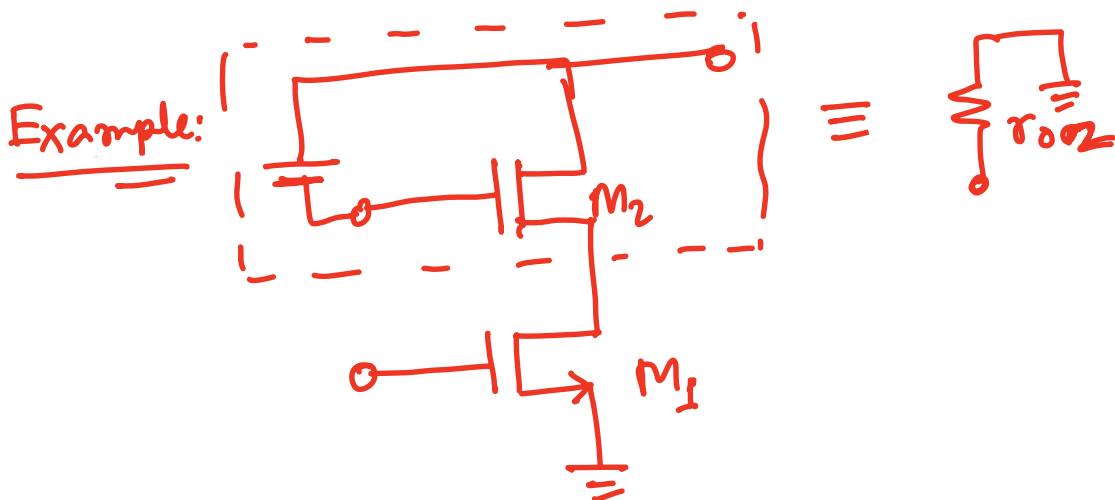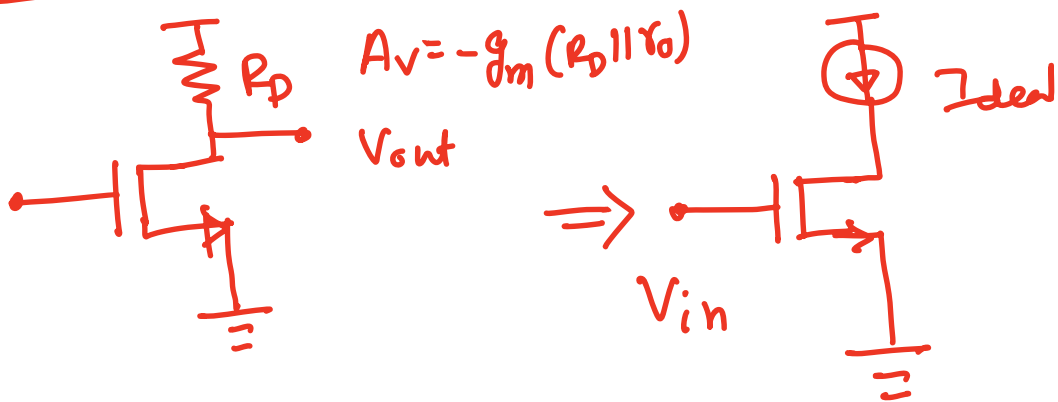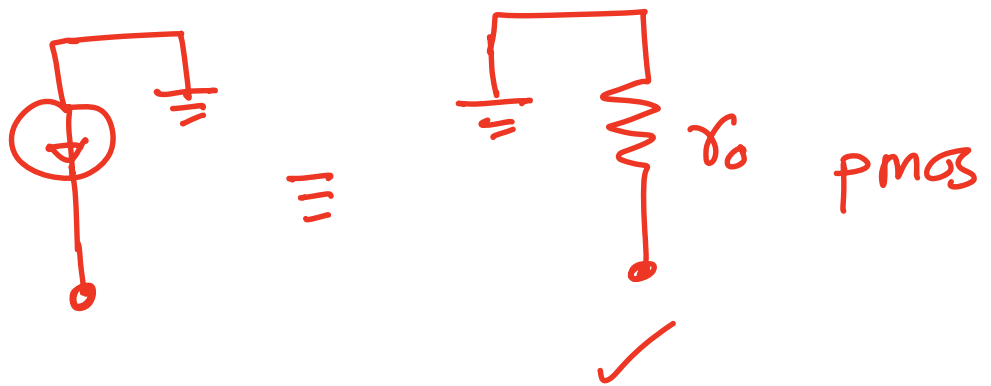

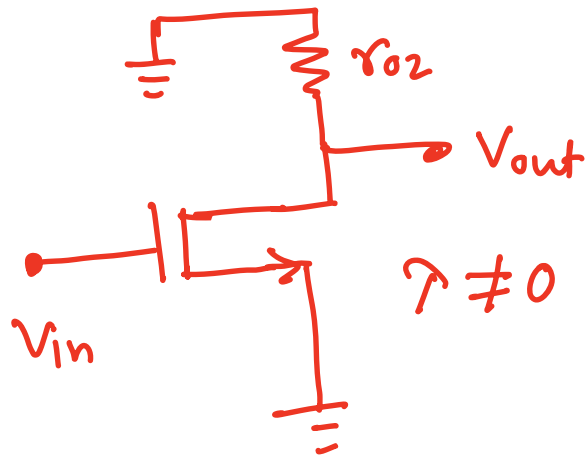

$$A_v = -g_{m1} r_{o2} \parallel r_{o1}$$

Example 7.6